
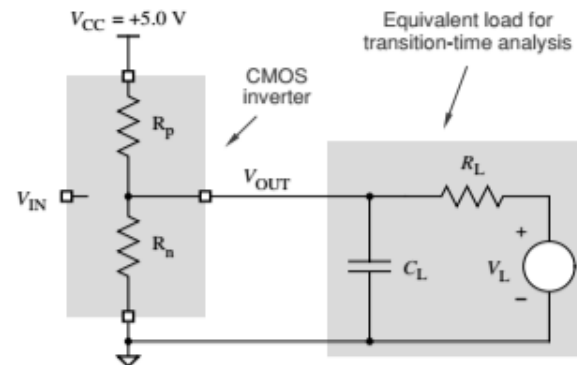





Electrónica III

Curso 2021



Comportamiento Dinámico

Rise and Fall time

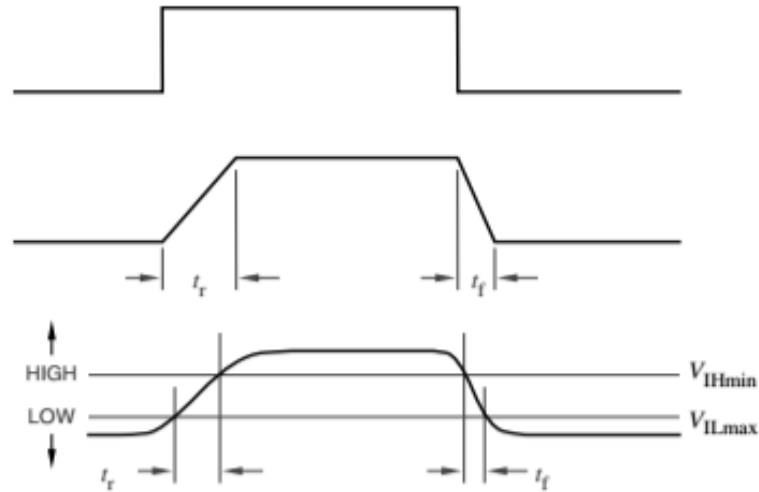

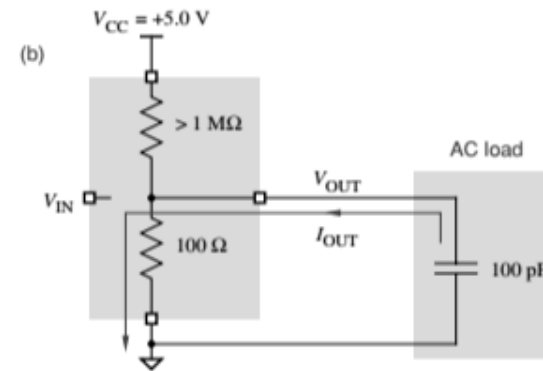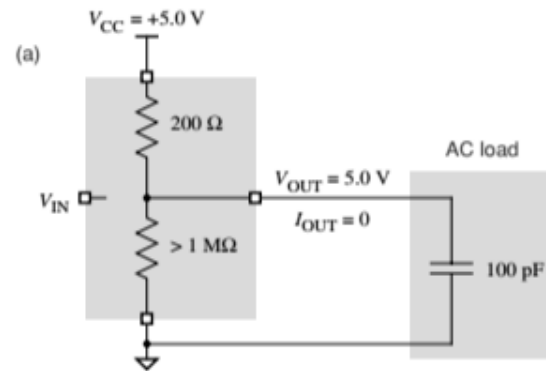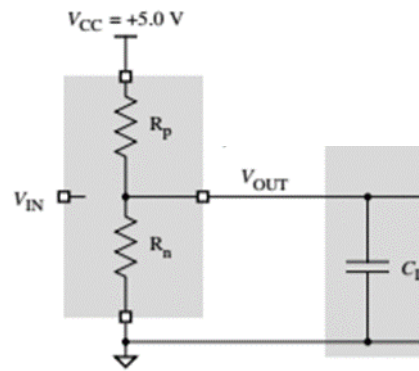

R_p	R_n
200 Ω	> 1 MΩ
> 1 MΩ	100 Ω

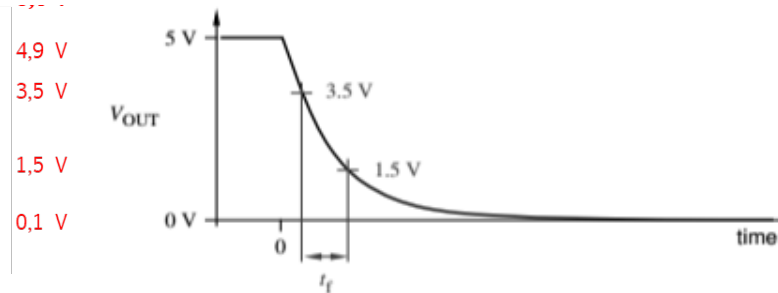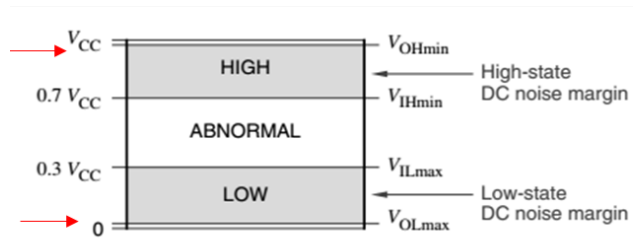

$$\begin{aligned}
 V_{OUT} &= V_{CC} \cdot e^{-t/(R_n C_L)} \\
 &= 5.0 \cdot e^{-t/(100 \cdot 100 \cdot 10^{-12})} \text{ V} \\
 &= 5.0 \cdot e^{-t/(10 \cdot 10^{-9})} \text{ V}
 \end{aligned}$$




$$t = -R_n C_L \cdot \ln \frac{V_{OUT}}{V_{CC}} = -10 \cdot 10^{-9} \cdot \ln \frac{V_{OUT}}{5.0}$$

$$t_{3.5} = 3.57 \text{ ns}$$



$$t_{1.5} = 12.04 \text{ ns}$$

$$t_f = t_{1.5} - t_{3.5} = 12.04 \text{ ns} - 3.57 \text{ ns} = 8.47 \text{ ns}$$
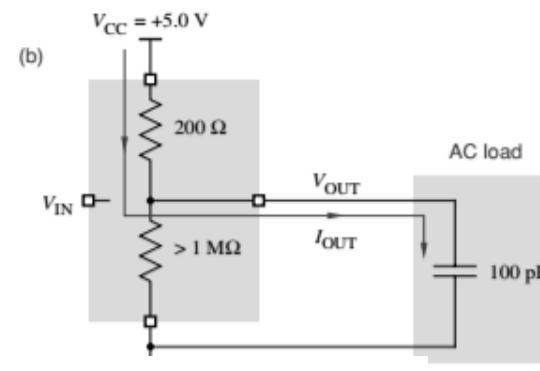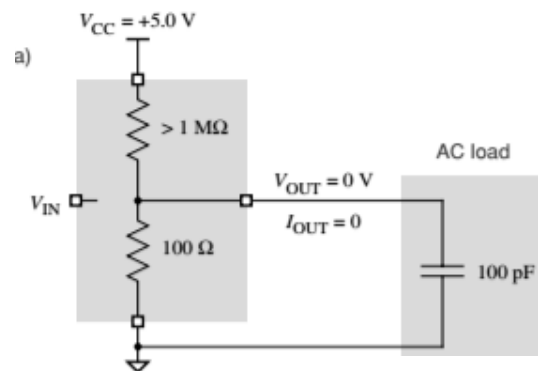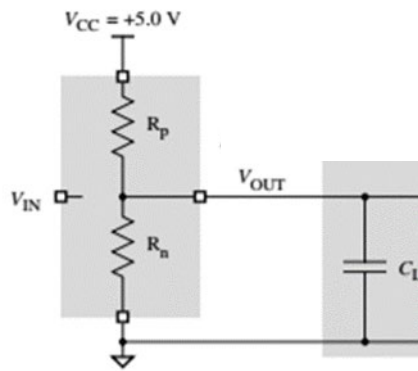
$$R_n \times C_L = 100 \times 100 \times 10^{-12} = 10 \times 10^{-9} = 10 \text{ ns}$$



R_p	R_n
200Ω	$> 1 \text{ M}\Omega$
$> 1 \text{ M}\Omega$	100Ω

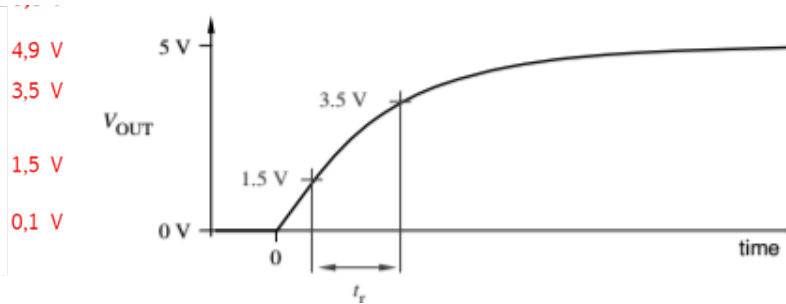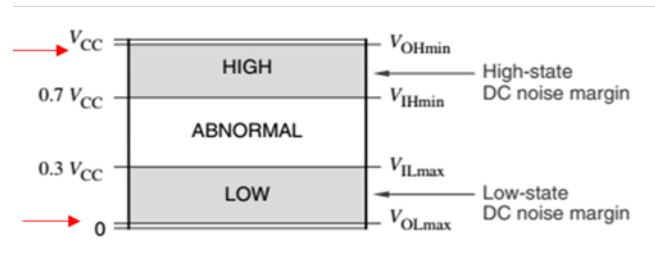

$$V_{OUT} = V_{CC} \cdot (1 - e^{-t/(R_p C_L)})$$

$$= 5.0 \cdot (1 - e^{-t/(200 \cdot 100 \cdot 10^{-12})}) \text{ V}$$

$$= 5.0 \cdot (1 - e^{-t/(20 \cdot 10^{-9})}) \text{ V}$$

$$t = -RC \cdot \ln \frac{V_{CC} - V_{OUT}}{V_{CC}}$$

$$= -20 \cdot 10^{-9} \cdot \ln \frac{5.0 - V_{OUT}}{5.0}$$


$$t_{1.5} = 7.13 \text{ ns}$$

$$t_{3.5} = 24.08 \text{ ns}$$

$$T_r = t_{3.5} - t_{1.5} = 24.08 \text{ ns} - 7.13 \text{ ns} = 16.95 \text{ ns}$$

$$R_p \times C_L = 200 \times 100 \times 10^{-12} = 20 \times 10^{-9} \text{ ns}$$


Propagation time

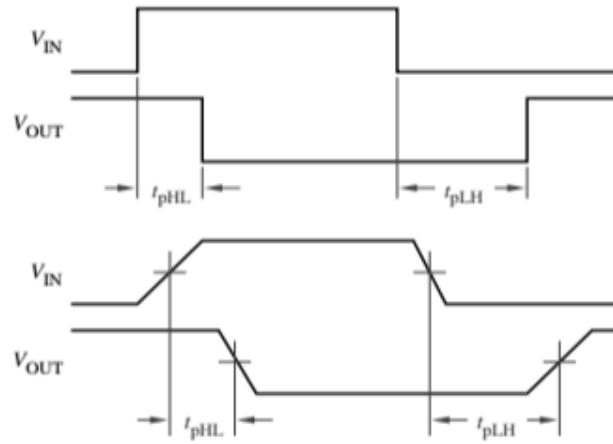


AC CHARACTERISTICS ($C_L = 50 \text{ pF}$, Input $t_r = t_f = 6 \text{ ns}$)

Symbol	Parameter	V_{CC} (V)	Guaranteed Limit			Unit
			-55 to 25°C	±85°C	±125°C	
t_{PLH} , t_{PHL}	Maximum Propagation Delay, Input A or B to Output Y (Figures 1 and 2)	2.0 3.0 4.5 6.0	75 30 15 13	95 40 19 16	110 55 22 19	ns
t_{TLH} , t_{THL}	Maximum Output Transition Time, Any Output (Figures 1 and 2)	2.0 3.0 4.5 6.0	75 27 15 13	95 32 19 16	110 36 22 19	ns
C_{in}	Maximum Input Capacitance		10	10	10	pF

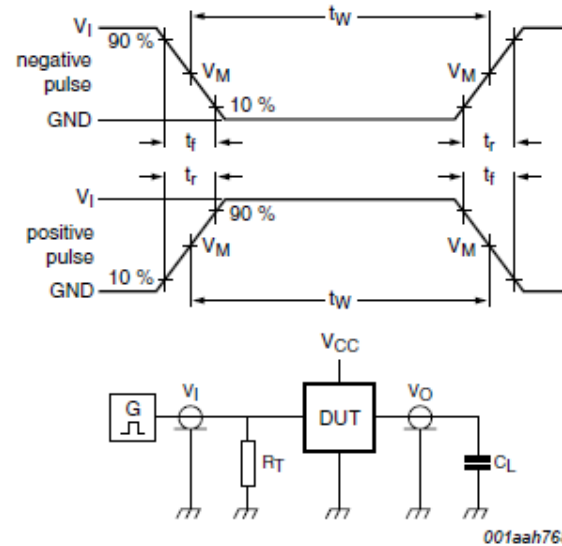NOTE: For propagation delays with loads other than 50 pF, and information on typical parametric values, see Chapter 2 of the ON Semiconductor High-Speed CMOS Data Book (DL129/D).



Potencia Consumida

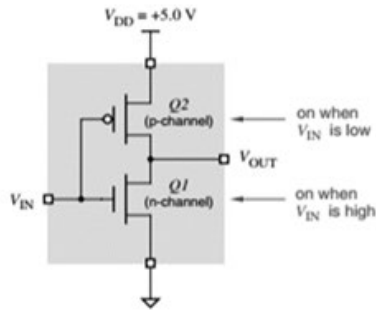

	$V_{CC} = 5.0 \text{ V}$	$V_{DD} = 5.0 \text{ V}$	V_{OUT}	C_{pd}
C_{pd}	No load, $T_A = 25^\circ\text{C}$		20	pF

$$P_{TG} = C_{PD} \cdot V_{CC}^2 \cdot f$$

$$f = 1 \text{ MHz}$$

$$V_{CC} = 5 \text{ V}$$

$$C_{PD} = 20 \text{ pF}$$

$$P_{TG} = 20 \text{ pF} \cdot 5^2 \cdot 1 \text{ MHz} = 0,5 \text{ mW}$$

$$P_{LG} = C_L \cdot V_{CC}^2 \cdot f$$

$$P_{DG} = P_{TG} + P_{LG} = C_{PD} \cdot V_{CC}^2 \cdot f + C_L \cdot V_{CC}^2 \cdot f$$

$$P_{DG} = P_{TG} + P_{LG} = (C_{PD} + C_L) \cdot V_{CC}^2 \cdot f$$

$$C_L = 10 \text{ pF}$$

$$P_{DG} = P_{TG} + P_{LG} = (20 \text{ pF} + 10 \text{ pF}) \cdot 5^2 \cdot 1 \text{ MHz} = 0,75 \text{ mW}$$

$$P_{\text{integrado}} = P_{DG} \cdot 4 = 0,75 \text{ mW} \cdot 4 = 3 \text{ mW}$$

Potencia Interna

Potencia en la carga


Potencia Total x Gate

Potencia Total x Integrado

I_{CC}	DC Supply Current, V_{CC} and GND Pins	± 50	mA
P_D	Power Dissipation in Still Air, SOIC Package† TSSOP Package†	500 450	mW



Potencia Consumida

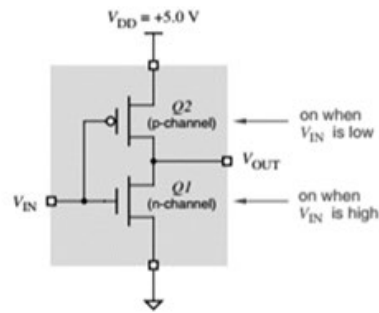

	$V_{CC} = 3.3 \text{ V}$	$V_{CC} = 1.8 \text{ V}$	
C_{pd}	Power dissipation capacitance per gate No load, $T_A = 25^\circ\text{C}$	20	pF

$$P_{TG} = C_{PD} \cdot V_{CC}^2 \cdot f$$

$$f = 1 \text{ MHz}$$

$$V_{CC} = 3,3 \text{ V}$$

$$C_{PD} = 20 \text{ pF}$$

$$P_{TG} = 20 \text{ pF} \cdot 3,3^2 \cdot 1 \text{ MHz} = 0,21 \text{ mW}$$

$$P_{LG} = C_L \cdot V_{CC}^2 \cdot f$$

$$P_{DG} = P_{TG} + P_{LG} = C_{PD} \cdot V_{CC}^2 \cdot f + C_L \cdot V_{CC}^2 \cdot f$$

$$P_{DG} = P_{TG} + P_{LG} = (C_{PD} + C_L) \cdot V_{CC}^2 \cdot f$$

$$C_L = 10 \text{ pF}$$

$$P_{DG} = P_{TG} + P_{LG} = (20 \text{ pF} + 10 \text{ pF}) \cdot 3,3^2 \cdot 1 \text{ MHz} = 0,33 \text{ mW}$$

$$P_{CHIP} = P_{DG} \cdot 4 = 0,33 \text{ mW} \cdot 4 = 1,3 \text{ mW}$$

$$P_{TG} = C_{PD} \cdot V_{CC}^2 \cdot f$$

$$f = 1 \text{ MHz}$$

$$V_{CC} = 1,8 \text{ V}$$

$$C_{PD} = 20 \text{ pF}$$

$$P_{TG} = 20 \text{ pF} \cdot 1,8^2 \cdot 1 \text{ MHz} = 0,06 \text{ mW}$$

$$P_{LG} = C_L \cdot V_{CC}^2 \cdot f$$

$$P_{DG} = P_{TG} + P_{LG} = C_{PD} \cdot V_{CC}^2 \cdot f + C_L \cdot V_{CC}^2 \cdot f$$

$$P_{DG} = P_{TG} + P_{LG} = (C_{PD} + C_L) \cdot V_{CC}^2 \cdot f$$

$$C_L = 10 \text{ pF}$$

$$P_{DG} = P_{TG} + P_{LG} = (20 \text{ pF} + 10 \text{ pF}) \cdot 1,8^2 \cdot 1 \text{ MHz} = 0,097 \text{ mW}$$

$$P_{CHIP} = P_{DG} \cdot 4 = 0,097 \text{ mW} \cdot 4 = 0,4 \text{ mW}$$

I_{CC}	DC Supply Current, V_{CC} and GND Pins	± 50	mA
P_D	Power Dissipation in Still Air, SOIC Package† TSSOP Package†	500 450	mW



Consideraciones en Conmutación



Características de una pista de Circuito Impreso

Inductancia = 10 nH por pulgada

Resistencia = 10 mΩ por pulgada

Capacidad = 1 pF por pulgada

Capacidad de Entrada por Pin : $C_{in} = 10 \text{ pF}$

Frecuencia de Operación : Giga Hertz

Tensión de Operación: 5 Volt – 3,3 Volt – 1,8 Volt

		0.0	13	10	19	
C_{in}	Maximum Input Capacitance		10	10	10	pF

$$V = L \cdot \frac{dI}{dt}$$

$$\left(\frac{dI}{dt}\right)_{\text{Max-resistor}} = \frac{\Delta V}{T_t} \cdot \frac{1}{R}$$

R : Resistencia de Carga

ΔV = Tensión de conmutación

T_t : Tiempo de Transición (t_r o t_f , el menor de ambos)

Symbol	Parameter	V _{CC} (V)	Guaranteed Limit			Unit
			-55 to 25°C	±85°C	±125°C	
t_{TLH} , t_{THL}	Maximum Output Transition Time, Any Output (Figures 1 and 2)	2.0	75	95	110	ns
		3.0	27	32	36	
		4.5	15	19	22	
		6.0	13	16	19	

$$\left(\frac{dI}{dt}\right)_{\text{Max-resistor}} = \frac{\Delta V}{T_t} \cdot \frac{1}{R}$$

$$R = 1 \text{ K}\Omega$$

$$\Delta V = 5 \text{ Volt}$$


$$T_t = 15 \text{ ns}$$

$$= 5 \text{ V} / (15 \text{ ns} \cdot 1 \text{ K}\Omega) = 3,3 \cdot 10^5 \text{ A/s}$$

Si lo aplico a mi fórmula

$$V = L \cdot \frac{dI}{dt}$$
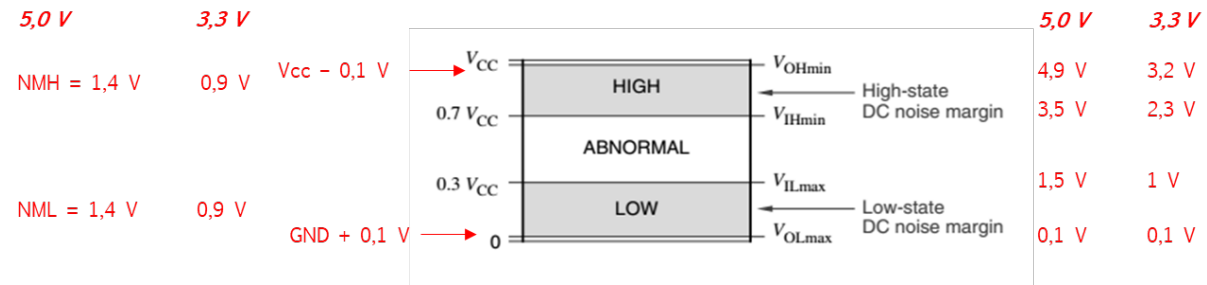
$$V = 10 \cdot 10^{-9} \cdot 3,3 \cdot 10^5 = 3,3 \text{ mV}$$



Que pasa si

$$R = 250 \Omega$$

$$\Delta V = 5 \text{ Volt}$$

$$T_t = 1 \text{ ns}$$

$$= 5 \text{ V} / (1 \text{ ns} \cdot 250 \Omega) = 20 \cdot 10^6 \text{ A/s}$$

$$V = 10 \cdot 10^{-9} \times 20 \cdot 10^6 = 200 \text{ mV}$$

Supongamos que trabajamos en 3,3 Volt

$$R = 250 \Omega$$

$$\Delta V = 3,3 \text{ Volt}$$

$$T_t = 1 \text{ ns}$$

$$= 3,3 \text{ V} / (1 \text{ ns} \cdot 250 \Omega) = 13,2 \cdot 10^6 \text{ A/s}$$

$$V = 10 \cdot 10^{-9} \times 13,2 \cdot 10^6 = 132 \text{ mV}$$

Finalmente en 1,8 Volt

$$R = 250 \Omega$$

$$\Delta V = 1,8 \text{ Volt}$$

$$T_t = 1 \text{ ns}$$

$$= 1,8 \text{ V} / (1 \text{ ns} \cdot 250 \Omega) = 7,2 \cdot 10^6 \text{ A/s}$$

$$V = 10 \cdot 10^{-9} \times 7,2 \cdot 10^6 = 72 \text{ mV}$$

Ground Bounce

$$\left(\frac{dI}{dt}\right)_{\text{Max-capacitor}} = \frac{1.52 \Delta V}{T_t^2} \cdot C$$

A modo de ejemplo:


$$C = 50 \text{ pF}$$

$$\Delta V = 5 \text{ Volt}$$

$$T_t = 5 \text{ ns}$$

$$= (1.52 \cdot 5 \text{ V} / (5 \text{ ns})^2) \cdot 50 \text{ pF} = 1.52 \cdot 10^7 \text{ A/s}$$
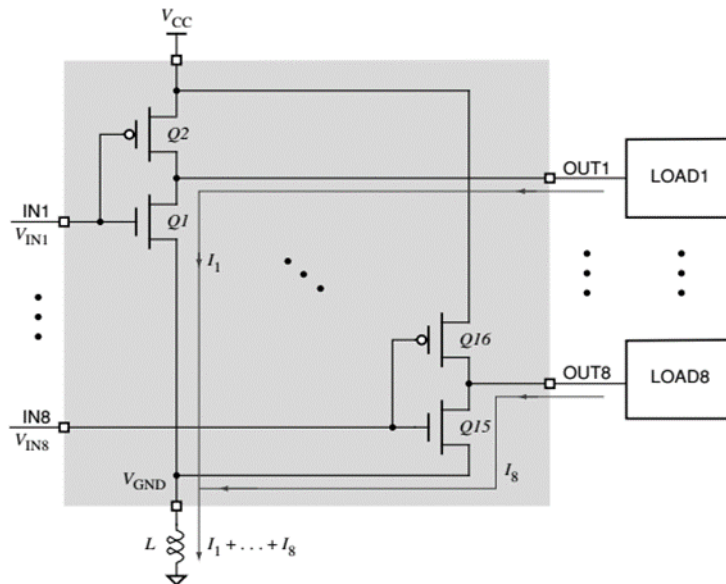
$$V = 10 \cdot 10^{-9} \times (1.52 \cdot 10^7) = 152 \text{ mV}$$




5,0 V

NMH = 1,4 V

3,3 V

0,9 V

$V_{CC} - 0,1 \text{ V}$

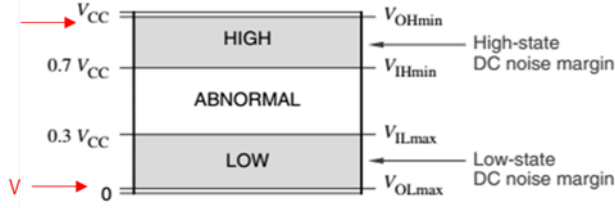

5,0 V

4,9 V

3,5 V

1,5 V

0,1 V

3,3 V

3,2 V

2,3 V

1 V

0,1 V


$$C = 50 \text{ pF}$$

$$\Delta V = 5 \text{ Volt}$$

$$T_t = 5 \text{ ns}$$

$$= (1.52 \cdot 5 \text{ V} / (5 \text{ ns})^2) \cdot 50 \text{ pF} = 1.52 \cdot 10^7 \text{ A/s}$$


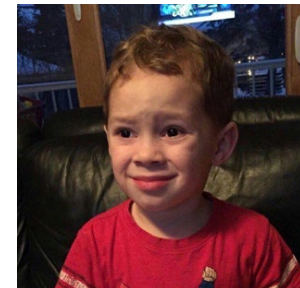
$$V = 10 \cdot 10^{-9} \times 8 \times (1.52 \cdot 10^7) = 1,216 \text{ V}$$




ITBA

Circuitos Especiales

Schmitt Trigger

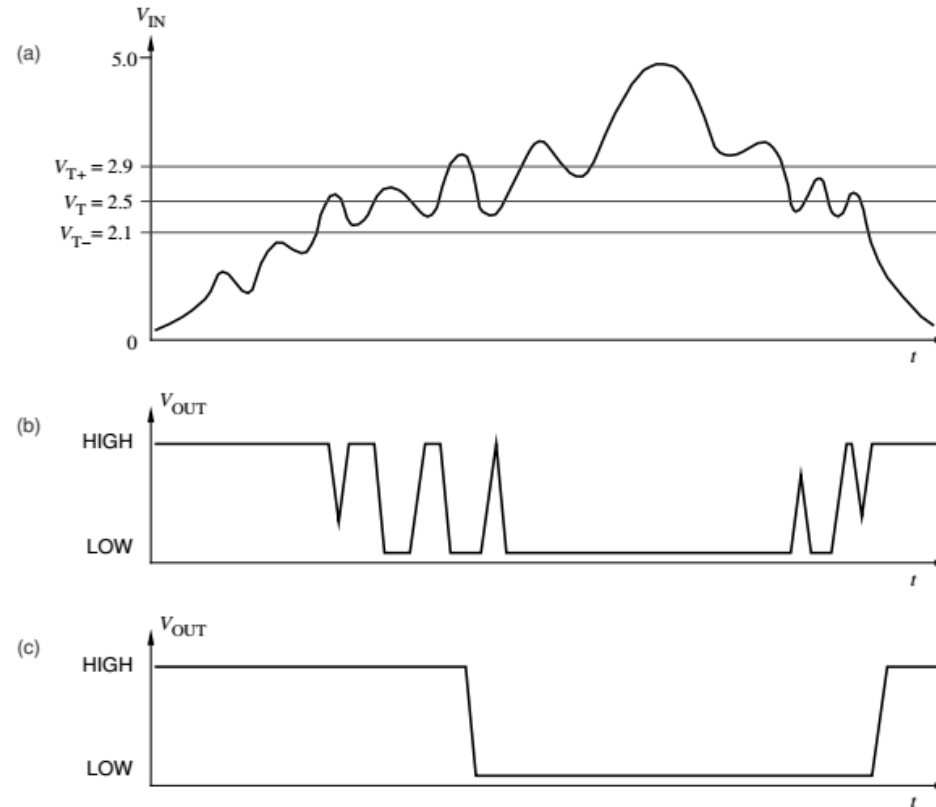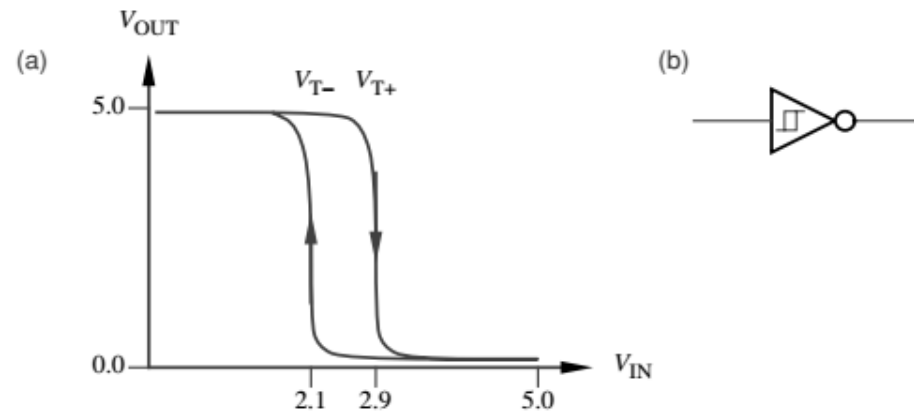


Three State

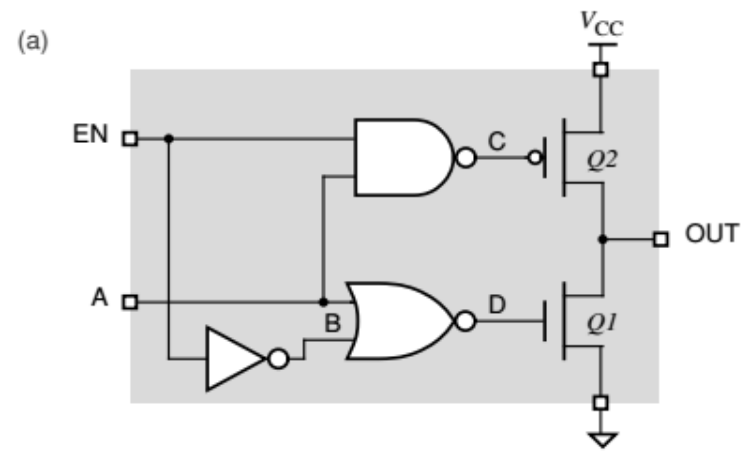


(b)


EN	A	B	C	D	$Q1$	$Q2$	OUT
L	L	H	H	L	off	off	Hi-Z
L	H	H	H	L	off	off	Hi-Z
H	L	L	H	H	on	off	L
H	H	L	L	L	off	on	H

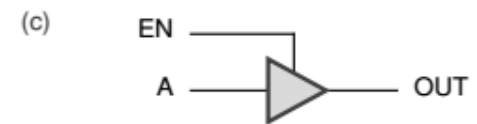

Three State


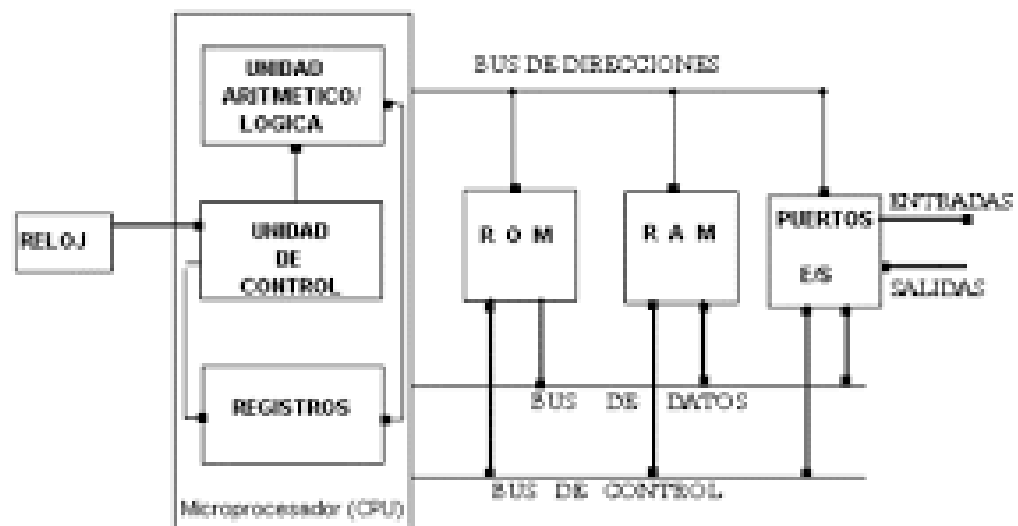


Open Drain

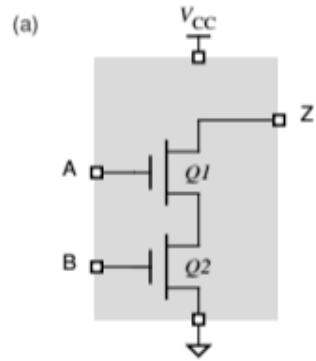

(b)

A	B	Q1	Q2	Z
L	L	off	off	open
L	H	off	on	open
H	L	on	off	open
H	H	on	on	L

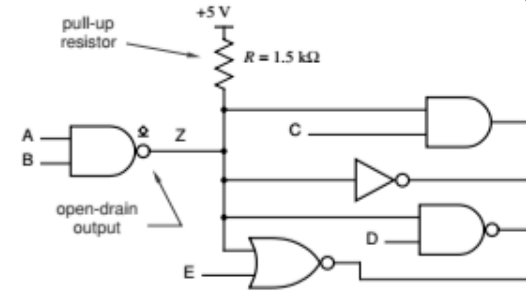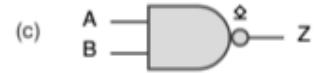



V_{OH}	Minimum High-Level Output Voltage	$V_{in} = V_{IH} \text{ or } V_{IL}$ $ I_{out} \leq 20\mu A$	2.0 4.5 6.0	1.9 4.4 5.9	1.9 4.4 5.9	1.9 4.4 5.9	V
		$V_{in} = V_{IH} \text{ or } V_{IL}$ $ I_{out} \leq 2.4mA$ $ I_{out} \leq 4.0mA$ $ I_{out} \leq 5.2mA$	3.0 4.5 6.0	2.48 3.98 5.48	2.34 3.84 5.34	2.20 3.70 5.20	

$$R_{pull\ up} = V_{cc} / I_{OLmax} = 5\ V / 4\ mA = 1250\ \Omega = 1,2\ K\Omega = 1K2$$

Si la capacidad de carga es $C_L = 100\ pF$

$$t_f = R_n \times C_L = 100\ \Omega \times 100\ pF = 10\ ns$$
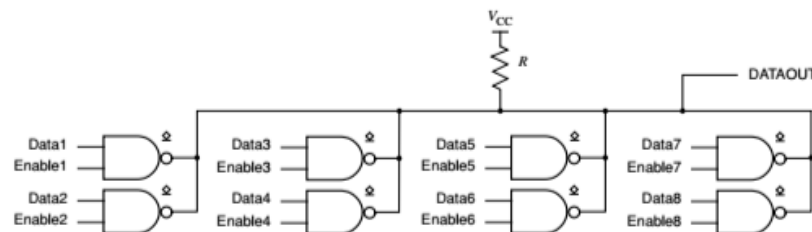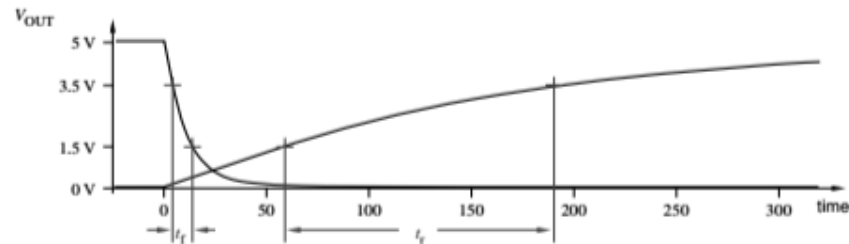
$$t_r = R_{pull\ up} \times C_L = 1,2\ K\Omega \times 100\ pF = 120\ ns$$



Familias CMOS

Description	Part	Symbol	Condition	Family			
				HC	HCT	AHC	AHCT
Typical propagation delay (ns)	'00	t_{PD}		9	10	3.7	5
	'138			18	20	5.7	7.6
Quiescent power-supply current (μA)	'00	I_{CC}	$V_{in} = 0$ or V_{CC}	2.5	2.5	5.0	5.0
	'138		$V_{in} = 0$ or V_{CC}	40	40	40	40
Quiescent power dissipation (mW)	'00		$V_{in} = 0$ or V_{CC}	0.0125	0.0125	0.025	0.025
	'138		$V_{in} = 0$ or V_{CC}	0.2	0.2	0.2	0.2
Power-dissipation capacitance (pF)	'00	C_{PD}		22	15	2.4	2.6
	'138	C_{PD}		55	51	13	14
Dynamic power dissipation (mW/MHz)	'00			0.55	0.38	0.06	0.065
	'138			1.38	1.28	0.33	0.35
Total power dissipation (mW)	'00		$f = 100$ kHz	0.068	0.050	0.031	0.032
	'00		$f = 1$ MHz	0.56	0.39	0.085	0.09
	'00		$f = 10$ MHz	5.5	3.8	0.63	0.68
	'138		$f = 100$ kHz	0.338	0.328	0.23	0.24
	'138		$f = 1$ MHz	1.58	1.48	0.53	0.55
	'138		$f = 10$ MHz	14.0	13.0	3.45	3.7

Description	Symbol	Condition	Family			
			HC	HCT	AHC	AHCT
LOW-level output current (mA)	I_{OLmaxC}	CMOS load	0.02	0.02	0.05	0.05
	I_{OLmaxT}	TTL load	4.0	4.0	8.0	8.0
LOW-level output voltage (V)	V_{OLmaxC}	$I_{out} \leq I_{OLmaxC}$	0.1	0.1	0.1	0.1
	V_{OLmaxT}	$I_{out} \leq I_{OLmaxT}$	0.33	0.33	0.44	0.44
HIGH-level output current (mA)	I_{OHmaxC}	CMOS load	-0.02	-0.02	-0.05	-0.05
	I_{OHmaxT}	TTL load	-4.0	-4.0	-8.0	-8.0
HIGH-level output voltage (V)	V_{OHminC}	$ I_{out} \leq I_{OHmaxC} $	4.4	4.4	4.4	4.4
	V_{OHminT}	$ I_{out} \leq I_{OHmaxT} $	3.84	3.84	3.80	3.80

Familias TTL

Description	Symbol	Family				
		74S	74LS	74AS	74ALS	74F
Maximum propagation delay (ns)		3	9	1.7	4	3
Power consumption per gate (mW)		19	2	8	1.2	4
LOW-level input voltage (V)	V_{ILmax}	0.8	0.8	0.8	0.8	0.8
LOW-level output voltage (V)	V_{OLmax}	0.5	0.5	0.5	0.5	0.5
HIGH-level input voltage (V)	V_{IHmin}	2.0	2.0	2.0	2.0	2.0
HIGH-level output voltage (V)	V_{OHmin}	2.7	2.7	2.7	2.7	2.7
LOW-level input current (mA)	I_{ILmax}	-2.0	-0.4	-0.5	-0.2	-0.6
LOW-level output current (mA)	I_{OLmax}	20	8	20	8	20
HIGH-level input current (μ A)	I_{IHmax}	50	20	20	20	20
HIGH-level output current (μ A)	I_{OHmax}	-1000	-400	-2000	-400	-1000



Inputs		output
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

